
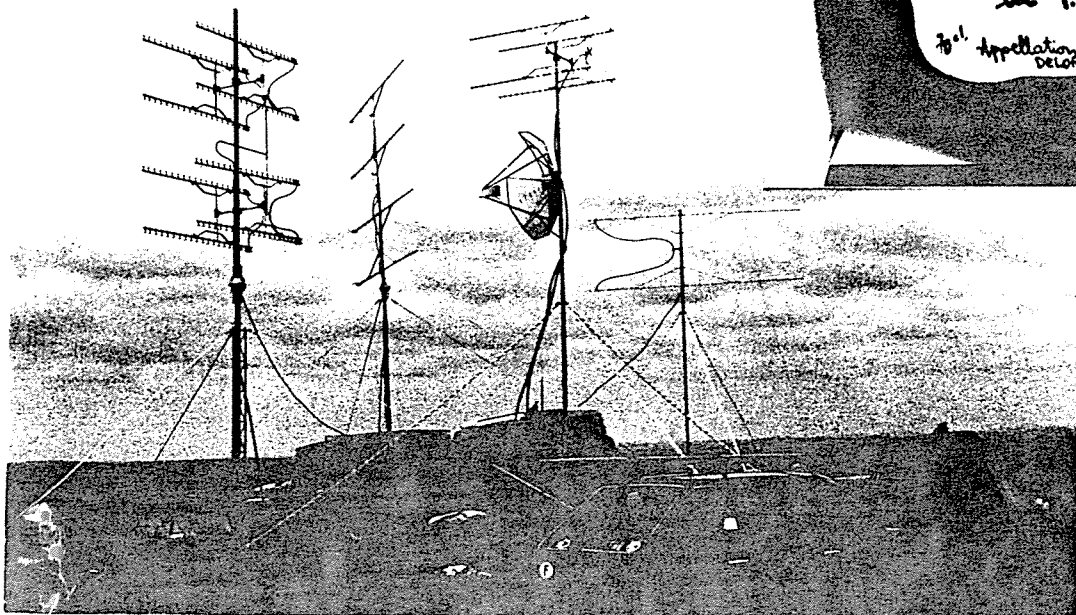



HURC INFOS

N°30 FEVRIER 88

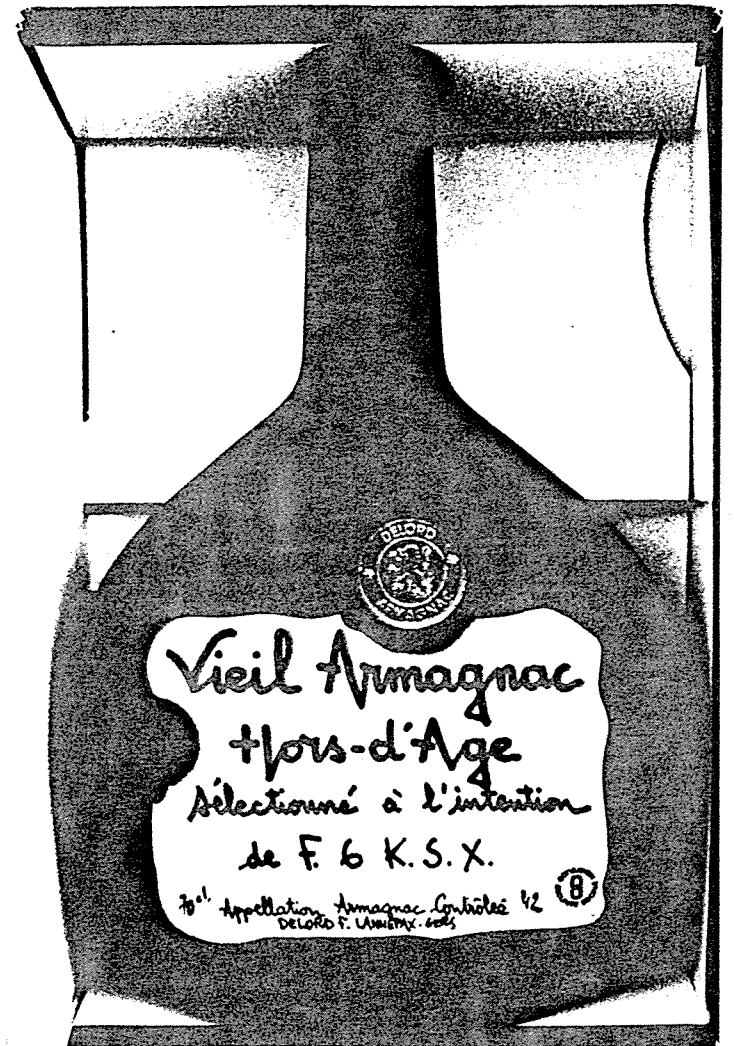


La reproduction de tout document est *strictement* interdite même pour usage personnel. Le contrevenant s'expose au paiement de quatre tournées de bière de qualité supérieure pour préjudice moral.

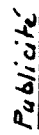Il paraîtrait que la joyeuse bande des suisses (HB9SAX,CVC,RDB etc) envisage une expédition en XH cet été (juillet ?)



**SUR MESURE
OU
CATALOGUE**

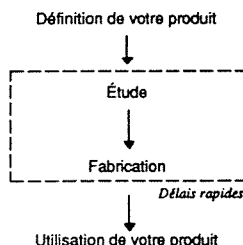

Amplificateurs hyperfréquence jusqu'à 20 GHz.

- Amplificateurs linéaires de puissance et à large bande.
- Amplificateurs à faible bruit.
- Amplificateurs de puissance en impulsions.
- Amplificateurs à large bande pour impulsions.
- Amplificateurs pour télévision.

Sources hyperfréquence jusqu'à 20 GHz.

- V.C.O.
- Oscillateurs à résonateur diélectrique.
- Synthétiseurs.

Systèmes et sous-ensembles sur spécification client.

Liaisons sur fibre optique à très large bande.

Composants.

- * Filtres, coupleurs, atténuateurs, charges.

14, Rue Pierre Métairie - Z.A. Le Bel Air - 78120 RAMBOUILLET
Sari au capital de 220.000 F - RCS Versailles B 339 632 630 - ☎ (1) 30 41 07 37 - APE 2914 FAB

EDITO



Comme d'habitude personne n'a rien fait ! (mis a part Georges toujours aussi prolifique) Heureusement on a eu pas mal de littérature de DJGBV ; d'autant plus que la version améliorée des antennes est arrivée alors que le bulletin était déjà bien avancé - Si vous ne voulez pas que l'HURK ressemble toujours au prochain DUBUS il serait temps de vous réveiller !!

FREIT - février 88

FLEIT - février 88

X-Element Yagi fuer 70 cm (Neufassung 1.9.86) *

1. Design-Daten

DJ 9 BV 7/84

Wellenlaenge (λ) : 694 mm (f = 432,0 MHz)
 Elementlaengen,-abstaende : nach DL 6 WU berechnet

2. Mechanische Daten

Boom : 20x20x2 mm Al-Vierkantprofil (Square Alu boom)
 Elemente : 4 mm $\varnothing$, Al-Rundstab (welding rod 4 $\varnothing$)
 El.-Befestigung : Isoliert durch Nylon-Niete Heyman 61PR800000


Element	(Laenge) Laenge [mm]	(Distance) Abstand [mm]	(Position) Position [mm]	Bemerkung
R1..R4	400	---	0	Vierfach-Ref.
R	340	---	0	Einfach-Ref.
S	325	130	130	8 mm Durchm.
D1	308	55	185	
D2	304	125	310	
D3	300	150	460	
D4	297	175	635	
D5	295	195	830	
D6	292	210	1040	
D7	289	220	1260	
D8	285	230	1490	
D9	285	240	1730	
D10	285	250	1980	
D11	281	260	2240	
D12	281	270	2510	
D13	281	280	2790	
D14	278	280	3070	
D15	278	280	3350	
D16	278	280	3630	
D17	275	280	3910	
D18	275	280	4190	
D19	275	280	4470	
D20	272	280	4750	
D21	272	280	5030	7,25 Lambda
D22	272	280	5310	
D23	270	280	5590	*
D24	270	280	5870	8,5 Lambda *
D25	270	280	6150	
D26	267	280	6430	
D27	267	280	6710	
D28	267	280	6990	10 Lambda
D29	267	280	7270	
D30	264	280	7550	11 Lambda

x 29 El with 4rv Reflector (Diagram)

+ d; 9270-35-mit:

D24 - D30: 1/8" (3,17 mm) $\varnothing$ Alu

15+15+1
Alu boom

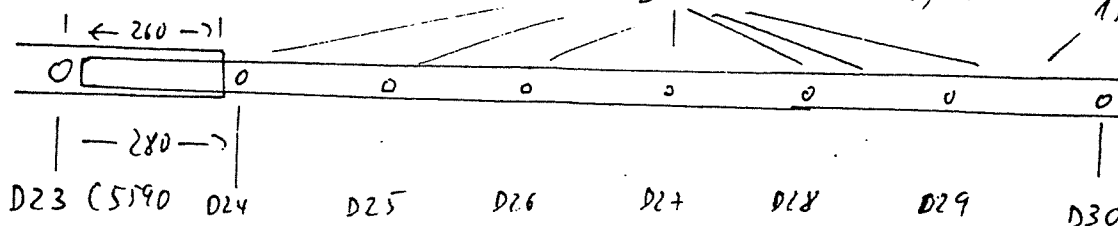


X-Element Yagi fuer 70 cm

DJ 9 BV 7/84

3. Aufbaudetails (Details)

3.1 Vierfach-Reflektor:

4-ref Reflector

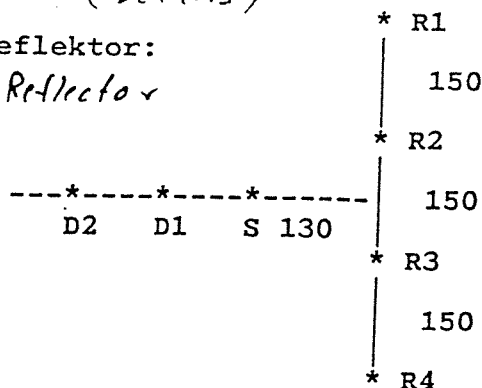

3.2 Dipol


Material:

8x1 Al-Rohr

(Alu-Tube)

Balun :


240 mm RG142 B/U, Teflon-Kabel, 50 Ohm

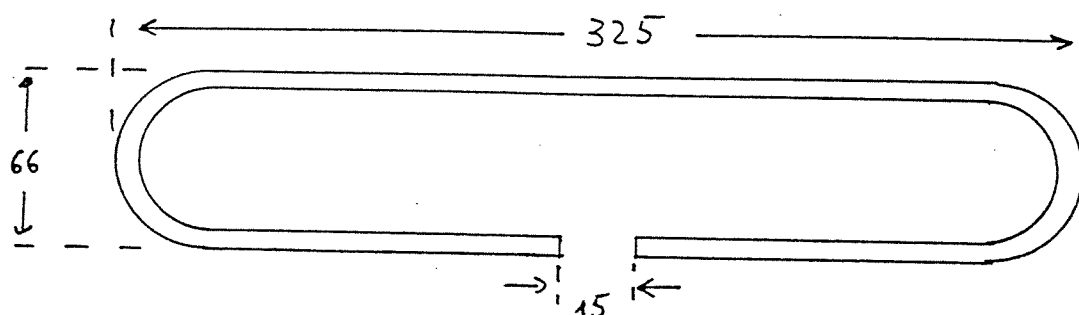

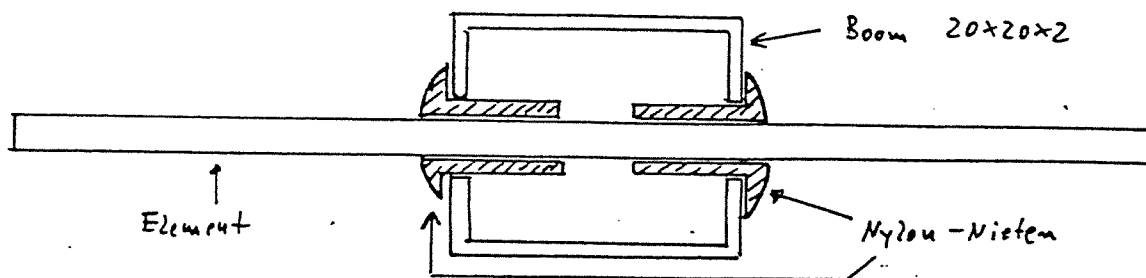3.3 Elementbefestigung (Isoliert, durch den Boom) (Isolated, through boom)

Elementhalter: Nylon-Niete Heymann 61PR800000





Elemente : Aluminiumstab, 4 mm Durchmesser









4. Elektrische Werte(Messungen/ Simulation) @ 432,5 MHz

Typ	Gain[dBD]	Phi-Hor [Grad]	Phi-Ver	D-Hor [m]	D-Ver
7,25	16,0	24,0	25,0	1,67	1,60
8,50	16,5	22,6	23,5	1,72	1,70
10,0	17,1	21,3	22,0	1,82	1,82
11,0	17,4	20,6	21,2	1,94	1,89

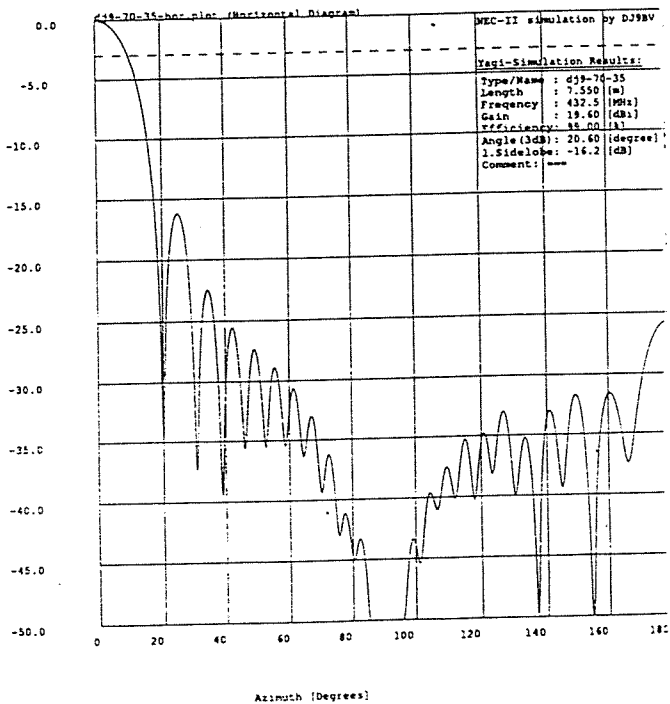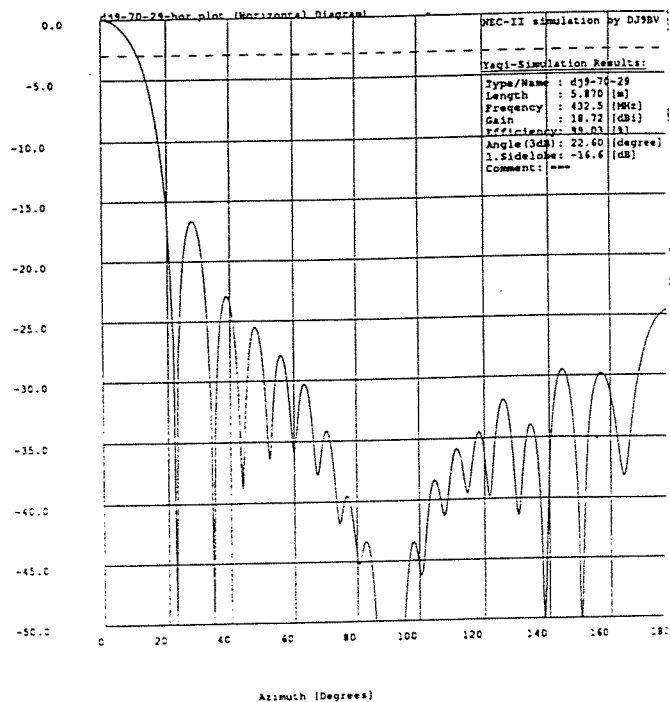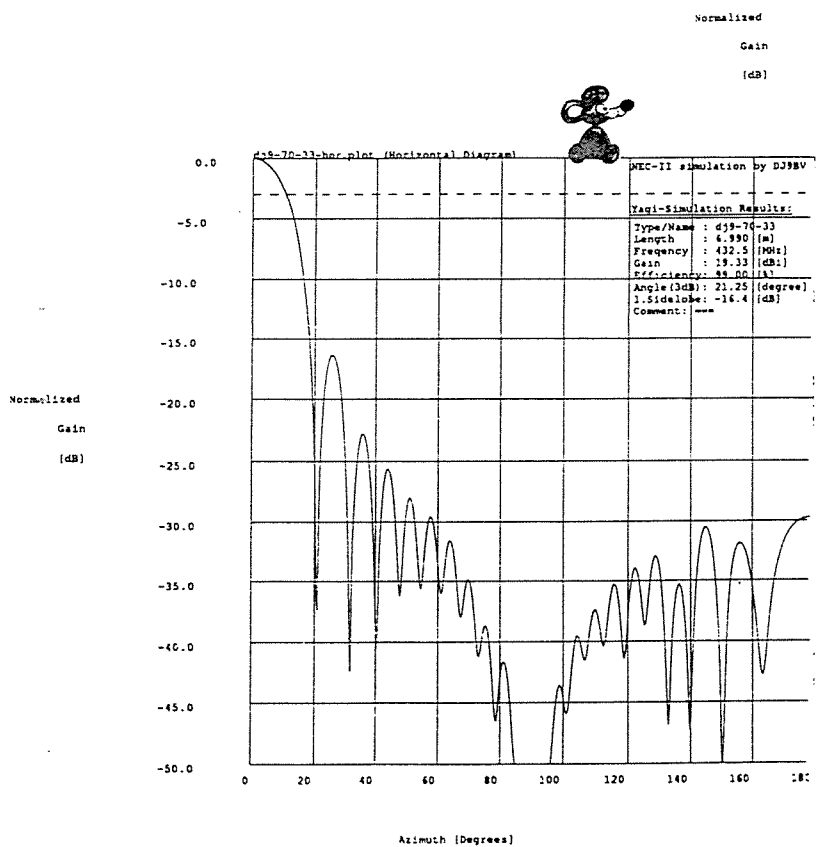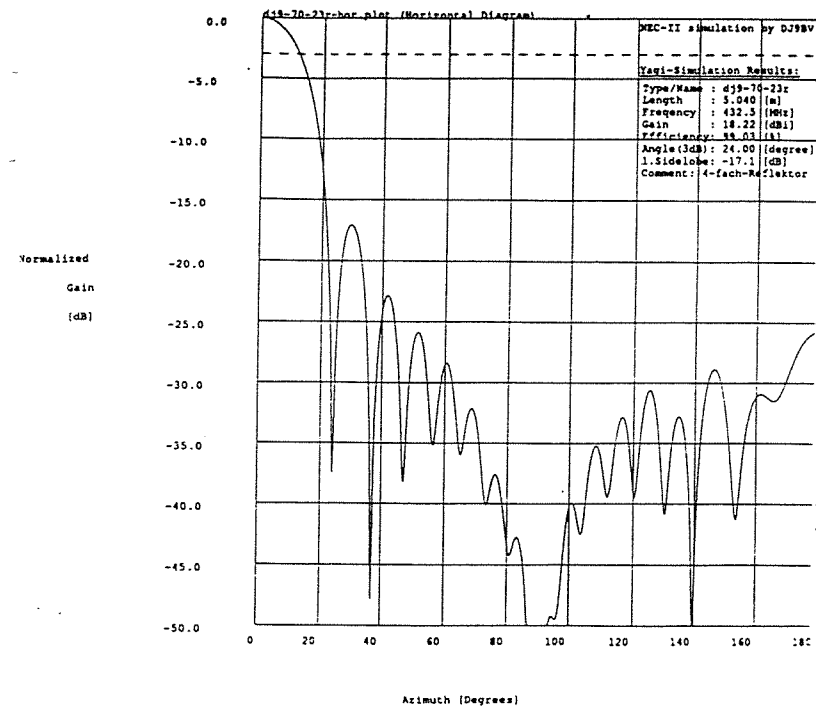Phi-Hor, Phi-Ver : 3 dB Oeffnungswinkel horizontal und vertikal (Angles)
 D-Hor, D-Ver : Optimale Stockungsabstaende (Optimal Stocking)



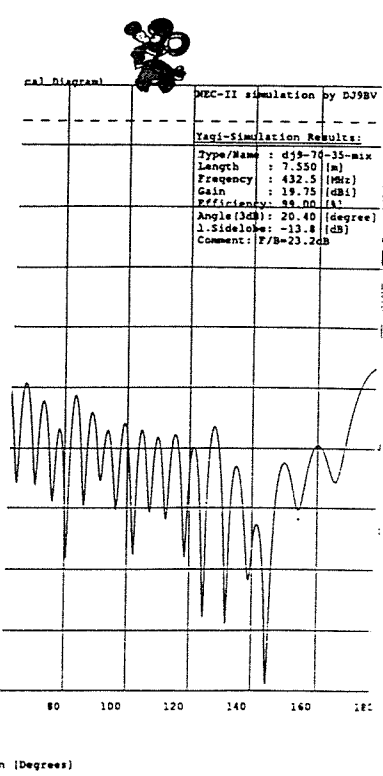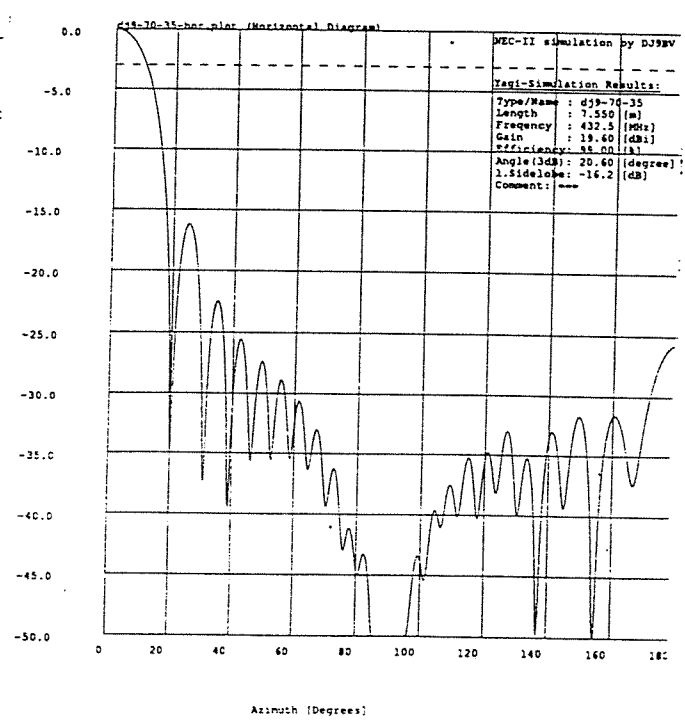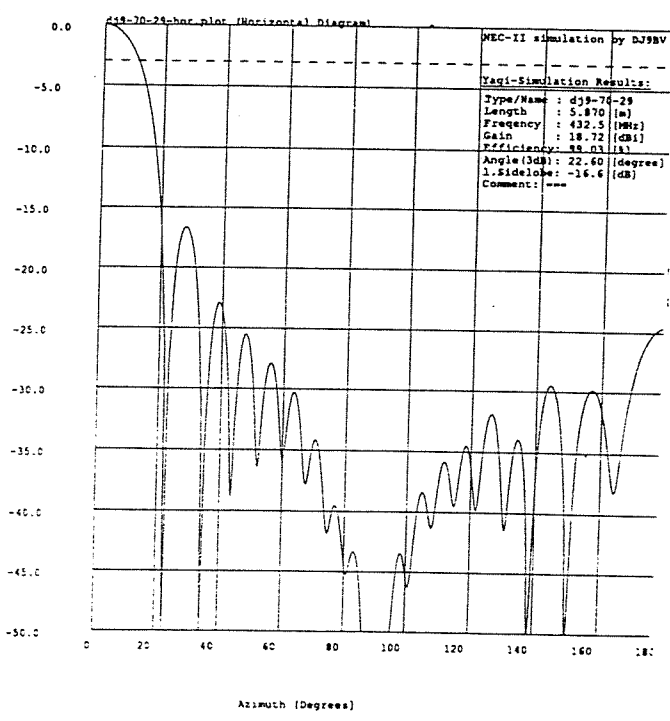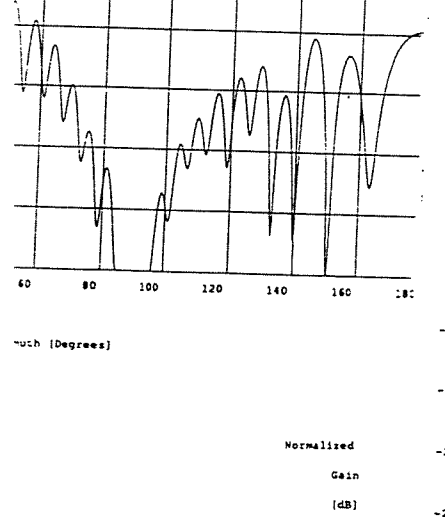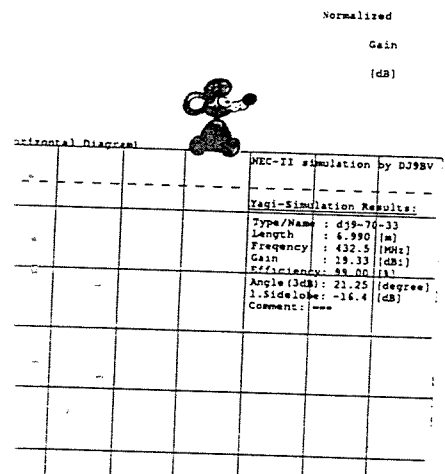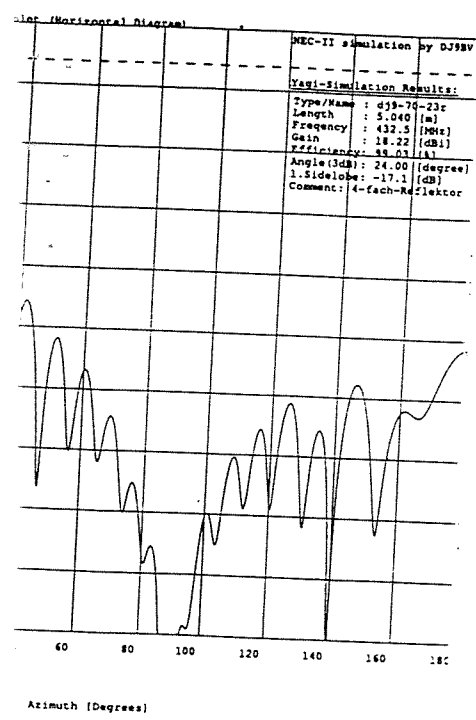

interessé pas mal de
 -gais ? Rainer

↓

→ 1 FLN,
 → translate
 into French
 REF.
 French in

LU POUR VOUS

MSN & CT DECEMBER 1987

DESIGN: Low-Power MIC Diode Doubler By Robert J. Hess, Loral Terracom

RF Design November 1987

Featured Technology — Designing Effective Two-Tone Intermodulation Distortion Test Systems

This article is a comprehensive description of a key RF test procedure: evaluation of intermodulation distortion (IMD) performance. In the high-ambient RF environments found today, good IMD dynamic range specifications are essential. — Manfred Bartz

Broadband Microwave Transistor Amplifier Design Using S-Parameters

In this article, the author takes us step-by-step through the design of a 1 to 2 GHz broadband amplifier, using S-parameter characterization. This rigorous examination illustrates in detail the basic principles of amplifier design. — Jackie L. Hughes

VHF Oscillators Using Microwave Integrated Circuits

demonstrates the use of common 50 ohm gain blocks in 50 and 250 MHz oscillators. — Wes Hayward

RF Design December 1987

Development of a New Direct VHF Synthesizer


Programmed Test Sources' new PTS-300, a signal synthesizer covering 0.1-300 MHz in 1 Hz steps, was developed to meet a specific set of performance requirements. This article provides insight into the engineering tasks required for the development of a new instrument by describing some of the concepts, design techniques and packaging methods developed by the PTS staff to create a synthesizer meeting their goals.

Featured Technology — S-Parameters of Wideband Op Amps and Buffers

High speed op amps and buffers are being increasingly used in RF and related analog applications. This article shows how these components' S-parameters can be measured, allowing engineers to use well-known RF design techniques with the DC-coupled, feedback-controlled technology of operational amplifiers. — Brian Mathews

RFI/EMC Corner — RF Radiation Hazards: Power Density Prediction for Communications Systems

Both public awareness and governmental regulation are increasing in the controversial area of non-ionizing radiation hazards. As a result, modeling and prediction of hazards will be required to determine whether a proposed communications system will exceed allowable levels. This article applies basic electromagnetic radiation models to ANSI standard C95.1-1982, the most widely used hazard guideline currently in use. — Gary A. Breed

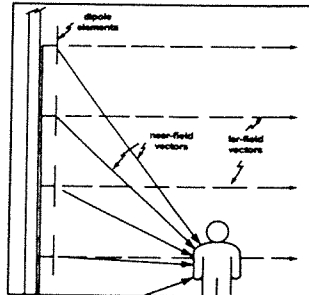

VHF COMMUNICATIONS 4/87

Roman Wesolowski, DJ 6 EP	5760 MHz Power-Amplifier using the YD 1060
Eugen Berberich, DL 8 ZX	VCOs using Semi-Rigid Cable Tuned Circuits
Dragoslav Dobričić, YU 1 AW	Pre-amplifier — Pros and Cons
Dragoslav Dobričić, YU 1 AW	Low-Noise 144 MHz Pre-Amplifier using Helical Tuned Circuits

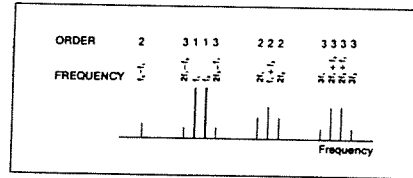


Figure 1. Second and Third Order Two-Tone Distortion Products.

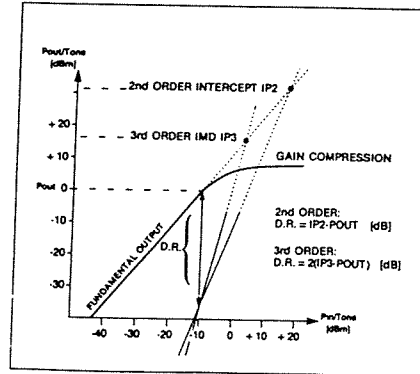


Figure 2. Distortion Dynamic Range Plot Depicting Intercept Points.

L'ONDE ELECTRIQUE janvier 1988

Analyse d'une micro-antenne à double fente à très large bande passante, par P. POEY, G. DUBOST, M. BAHAM et P.L. GUIGUE

Toute l'électronique Janvier 1988

Les résonateurs à ondes acoustiques de surface, les résonateurs diélectriques, par R. Besson.

Marteaux d'ingénieur CeKa

Tête forgée à faces polies. Manche en bois
Poids: 227 g

Code	U.d.V.	Prix
Commande 74-36972G	1	35,00

à métaux junior



Mais c'est nous qui nous sommes réunis pour ça

Cher OM, YL et SWL

Par la présente nous vous remercions pour l'intérêt que vous manifestez à l'activité de notre Association.

Par votre assistance technique, votre adhésion, vous nous avez permis de mettre en service le RI-élément essentiel des possibilités de communication entre tous les OM du département.

Nous souhaitons resserrer les liens et proposons une rencontre pique-nique pour le Dimanche 26 Juillet.

A ce jour le lieu n'est pas défini. Nous pensons choisir le centre du 07; que le site nous permette des liaisons Radio correctes la possibilité d'abri en cas de mauvais temps.

Des informations plus précises seront communiquées



Precision powermeter for 144-2320 MHz with automatic VSWR display

Copyright © 1987 by R. Bertelsmeier

Rainer Bertelsmeier

DJ9BV

Glücksburger Str. 20
2 Hamburg 50

1. Introduction

An accurate powermeter is an important piece of measurement equipment for each serious VHF/UHF-amateur. Commercial equipment is very expensive. Products designed for amateur use usually have insufficient quality.

The following article describes an electronic powermeter which in conjunction with commercially available precision directional couplers provides the following features:

- (1) Frequency range:
144 - 2320 MHz
- (2) Power range:
1,2-4000 (not usable) Watt @ 144 MHz
0,3-1000 (0,6-2000) Watt @ 432 MHz
0,03-100 (0,12-400) Watt @ 1296 MHz
0,01-40 (0,03-100) Watt @ 2320 MHz
with Directional Coupler EME2320A (EME2326A: Values in brackets)
- (3) Functions:
Power measurement
 - Forward-Backward-Power
 - PEP measurement (Peak power)
 - CW measurement (Average power)
 - 3 power ranges : 1,10,100
 Automatic VSWR-measurement (Built-in analog computer)
 - VSWR-Low : 1,0 - 2,0
 - VSWR-High: 1,0 - Infinite
- (4) Power supply:
NC-Accu (Max. 10 hours)
Mains 220 V (NC-Accu is charged)
- (5) Directional coupler:
Any suitable directional coupler can be used
Connection via 5-pin DIN-socket up to 20 m remote

2. Functional description of directional couplers

A directional coupler provides a directional sensitive coupling between a main coaxial line and a coupled coaxial line. Directional couplers with two coupled lines with reverse directional sensitivities provide an easy means to measure the forward and backward power on a coaxial line simultaneously (Figure 1). The coupled RF-Power on the coupled line can be rectified by RF-Detectors (i.e. Schottky rectifier) and the resultant DC-voltage can be indicated.

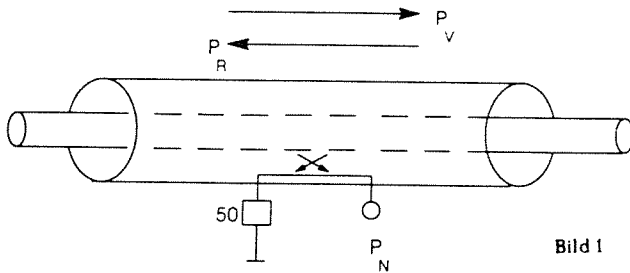


Bild 1

Directional coupler have certain quality properties:

- Coupling $K = \sqrt{\frac{P_n}{P_r}}$
- Isolation $I = \sqrt{\frac{P_n}{P_f}}$
- Directivity $D = \frac{K}{I}$

Directivity determines the ability of a directional coupler to differentiate between forward and reflected power on the main line. It limits the accuracy of the measurement of power and return loss ($RL = \sqrt{P_r/P_f}$). The VSWR can be calculated from the return loss RL by a simple equation.

The diagram of a coupled line (Figure 2) shows the two RF-voltages, which develop from the forward power and the reflected power. These two voltages add with their magnitude and phase:

$$U_N = \frac{U_V}{I} + \frac{U_R}{K} \text{ bzw. } U_N = \frac{1}{K} (U_F + D U_V)$$

With finite isolation the two voltages can add in phase or even cancel (phase is 180°). So a variable measurement error, which depends on the directivity and the current relative phase of forward and reflected wave on the main line, will be observed.

This fact can be observed by inserting a directional coupler at different positions on a coaxial line. The indicated VSWR will be a function of the position on the line, because the relative phase changes. If the measured return loss has the same magnitude as the directivity the measurement error reaches 100%. In this case the two resulting voltages on the coupled line $\frac{U_V}{I}$ und $\frac{U_R}{K}$ (Figure 2) have the same magnitude. Therefore they can add to zero or to twice their value dependent on their relative phase.

The directivity is the lower bound on the measurable return loss.

VSWR can be derived from return loss:

Equation(1):

$$VSWR = \frac{1+RL}{1-RL}$$

$$\text{mit } RL = \frac{|U_r|}{|U_f|}$$

Available VSWR-Meters, offered for amateur bands on VHF/UHF, have couplers of poor directivity. For example strip-line couplers or open lines provide directivities of not more than 20 dB.

Good couplers have a directivity of better than 30 dB. Examples of good couplers are the BIRD-43 and the couplers produced by EME.

Especially the couplers 2320A and 2326A of EME show an excellent value of directivity over a great frequency span (Figure 3).

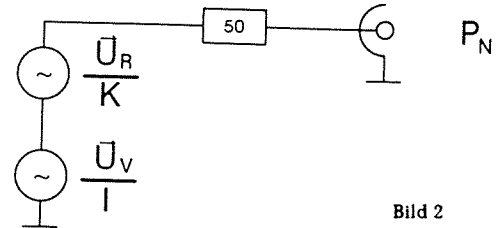


Bild 2

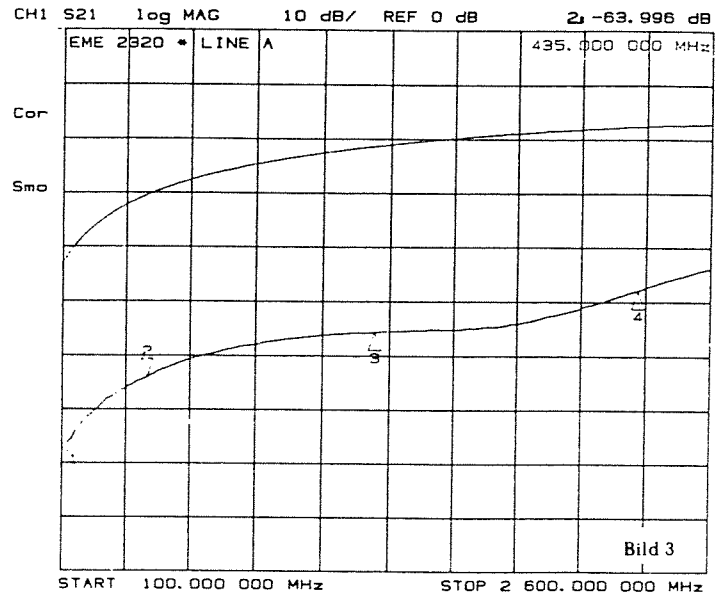


Bild 3

The following table displays the typical values:

Typical parameters EME2320A		
Frequency [MHz]	C [dB]	D [dB]
144	-37	35,5
432	-30	33,5
1296	-20	34
2320	-16	30,5

The following table indicates the influence of directivity on the measurement error:
Tabelle 1:

VSWR-measurement error @ directivity D					
True VSWR	RL [dB]	Measured VSWR (Minimum - Maximum)			
		D=33db	D=30dB	D=20db	
1.05	32.26	1.00 1.10	not measurable	not meas.	
1.10	26.44	1.05 1.15	1.03 1.17	not meas.	
1.15	23.13	1.10 1.20	1.08 1.23	not meas.	
1.20	20.83	1.15 1.26	1.13 1.28	not meas.	
1.25	19.08	1.19 1.31	1.17 1.33	1.02 1.54	
1.30	17.69	1.24 1.36	1.22 1.39	1.06 1.60	
1.40	15.56	1.34 1.47	1.31 1.49	1.14 1.73	
1.50	13.98	1.43 1.57	1.40 1.60	1.22 1.86	
1.60	12.74	1.53 1.68	1.50 1.71	1.30 1.99	
1.80	10.88	1.71 1.89	1.68 1.93	1.46 2.26	
2.00	9.54	1.90 2.10	1.86 2.15	1.61 2.53	
2.20	8.52	2.09 2.32	2.05 2.37	1.76 2.81	
2.40	7.71	2.28 2.53	2.23 2.59	1.91 3.10	
2.60	7.04	2.46 2.75	2.41 2.82	2.05 3.39	
2.80	6.49	2.64 2.97	2.58 3.04	2.19 3.69	
3.00	6.02	2.83 3.19	2.76 3.27	2.33 4.00	
3.50	5.11	3.28 3.74	3.20 3.84	2.67 4.81	
4.00	4.44	3.73 4.30	3.63 4.43	3.00 5.67	
4.50	3.93	4.18 4.86	4.06 5.02	3.31 6.59	
5.00	3.52	4.62 5.43	4.48 5.63	3.62 7.57	

(Remark:

The assumed values for directivity are characteristic values:

33db:Typical value for EME-2320A.

30db:Guaranteed value for EME-2320A and BIRD 43.

20db:Typical value for an "unspecified" coupler, i.e. amateur type equipment)

It can easily be concluded, that the quality of simple amateur type couplers is unsatisfactory even for low demands on accuracy. A directional coupler with a directivity of at least 30 dB is a mustfor measuring an VSWR under 1.2.

3. Powermeter construction

The use of a precision directional coupler a la BIRD or EME is one condition for a good power meter. A second one is the realisation of wide dynamic range RF-rectifiers with Schottky diodes. That's not an easy task, as can be seen in Figure 4. The dynamic range of simple detectors is very limited. A simple Schottky-detector ("Ohne Vorstrom") shows an dynamic range of only 20 dB

Such a small dynamic range is not sufficient to use the excellent directivity of 33 dB of an EME-coupler. So the RF-detectors limit the accuracy of VSWR measurement.

Sometimes different scales are provided to get rid of the unilinear detector. So you arrive with 12 scales for 4 bands and 3 power ranges per band! Second, because of the poor linearity, the minimum power, which is necessary for measurement of a certain VSWR is very large, because the diode on the reflected power line cannot detect small RF-power. So you need 1000 W = 60 dBm forward power at 432 MHz on the main line to develop 10 mW = 10 dBm on the reflected power line with a VSWR of 1.22 = 20 dB return loss on the main line (60 dBm power - 20 dB return loss - 30 dB coupling factor = + 10 dBm)!

A better solution is the linearisation of the Schottky detector by a small DC-current and the compensation of the ON-voltage of .2 Volts. A dynamic range of ca. 35 db is-achievable (see curve "mit Vorstrom" in Figure 4). Powers on the coupled lines down to - 5 dBm can be measured with 1 dB linearity and down to -15 dBm can be indicated.

This high dynamic range of the RF-detectors allows the following properties:

1. One scale for 3 power ranges (1,10,100) and all bands.
2. VSWR-measurements down to the directivity limitation (VSWR min = 1,045) even with small forward power.
3. Automatic VSWR-measurement and display by analog computation of the quotient of U_f und U_r over the full dynamic range.
4. Great linear display range for power (EME2320A-coupler)

144 MHz:1,2 - 4000 W
432 MHz:0,3 - 1000 W
1296 MHz:0,03 - 100 W
2320 MHz:0,01 - 40 W

The following table displays the minimum power for accurate VSWR-measurement:

Table 2:

Frequency [MHz]	Minimum forward power for VSWR-measurement Minimum power [W]		
	SWR=1,5(RL=14dB)	SWR=1,22(RL=20dB)	SWR=1,1(RL=26dB)
144	50	200	800
432	8	32	126
1296	0,8	3,2	13
2320	0,3	1,2	5

With forward power greater than the value in the table the resulting VSWR will be displayed accurate independent on the forward power. With forward power lower than the table value the displayed VSWR is "optimistic", i.e. the true return loss is only 3 dB less with even 1/10 of the minimum power.

4. Technical realisation

4.1. Linearisation of Schottky detectors

The Schottky diodes in the RF-detectors have a small ON-current of ca. 20 μ A. The small ON-voltage of 0.2 Volt is compensated by means of a subtracting operational amplifier, which subtracts the temperature sensitive voltage of an Si-diode in the right proportion.

4.2. VSWR-Computation

The two voltages U_f and U_r are input to an analog divider, which calculates the quotient of U_f and U_r , i.e. the return loss, over the full dynamic range of 35 dB. The scale of the display instrument reads directly VSWR or return loss. By weighing the reflected voltage by a factor of 3 a sensitive scale with VSWR=2.0 full scale is realized. The user can switch between "High" and "Low" VSWR scale.

4.3. PEP-power display

By virtue of a peak/hold circuit the peak envelope power can be displayed. The aquisition time is 5 msec and the hold time is about 4 sec. This feature is useful for tuning of PA's with morse code or voice.

HF-Kennlinien von Schottky-Dioden

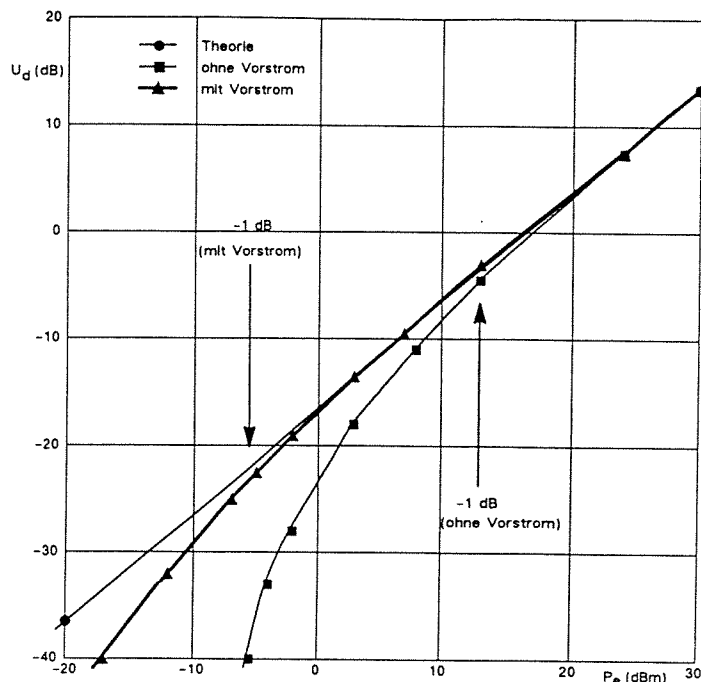


Bild 4

4.4. Power ranges and accuracy

For each frequency band a separate calibration is possible. Possibly different coupling factors for the two coupled lines can be tuned also. Because of the large dynamic range of the RF-detectors, the power range can be switched in three decades, i.e. over 30 dB full scale. The deviation from the quadratic relationship is less than 0.4 db over this range. That corresponds to an error of 9 %.

The smallest indicatable power is -45 dB from full scale.

The maximum power in each band depends on the coupling factor only. The power on the detector is limited to +30dBm. So the maximum power, which can be calibrated, is 30 dBm + coupling factor. However you have to care for the maximum power rating of the connectors also to determine the real usable maximum power. For the case of two different couplers from EME the resulting power limits are given above.

4.5. Power supply

The electronics are powered by 6 AA-size NC-batteries, which are charged if the instrument is connected to the mains. The battery operation is useful for nearly 10 hours before recharging. Charging current is very low (C/50), so no danger of overcharging exists. Built inverters and regulators eliminate any changes in the supply voltage.

DJ9BV (Copyright © 1987 by DJ9BV)

Wattmeter Vers.3

1/87

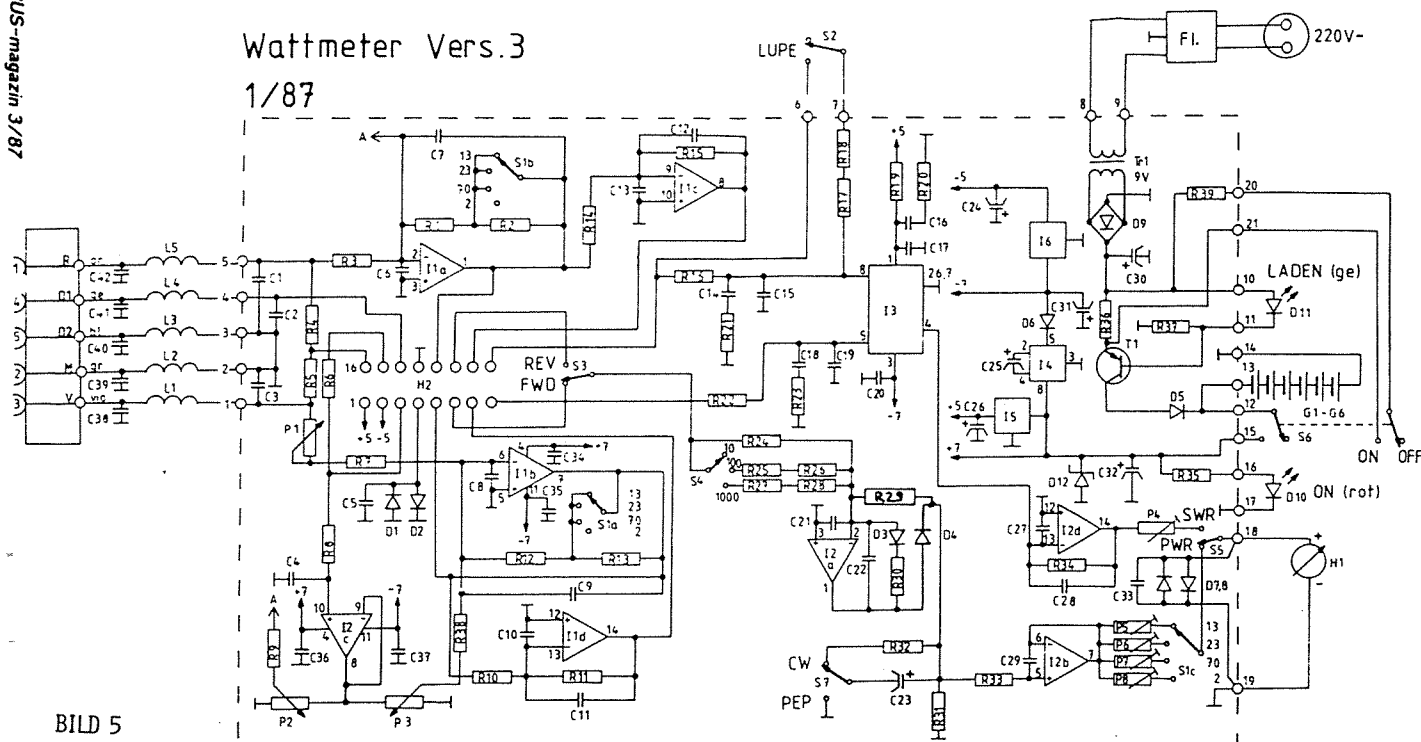


BILD 5

5. Operation

The front plate has switches for:

- Range: 1,10,100
- Mode: PEP/CW
- Meter: PWR/SWR
- Dir: FWD/REV
- Band: 2,70,23,13
- SWR: Low/High
- OFF: EIN/AUS

The scale of the display instrument has divisions for:

- P: Power (0,1 - 10 Watt)
- RL: Return loss (10 - 30 dB)
- VSWR: (Low: 1,0-2,0; High: 1,0 - Infinite)

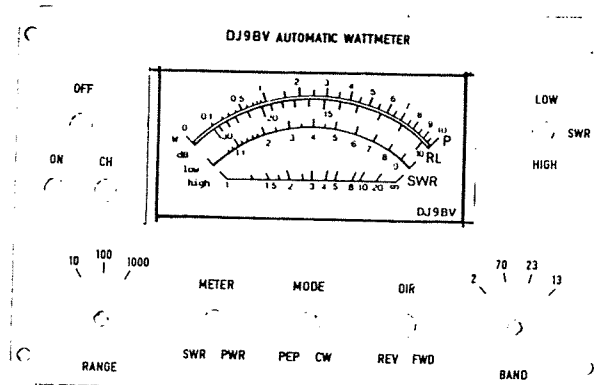


Bild 6

Two LED's show the state: The red one is for ON and the yellow one is illuminated during charging.

For power measurement the switch "METER" is switched to "PWR". The switch "DIR" selects between forward and reflected power. Switch "MODE" selects "PEP" or average value "CW" display.

If the meter switch is switched to "SWR", one can select two sensitivities for VSWR measurement with the SWR switch. In the "LOW" position the corresponding return loss can be read from the RL-scale (10-30db).

6. Calibration

The calibration procedure is covered in the construction documentation.

!

Si vous êtes sages je vous traduirai


le chapitre calibration (Dubus 3-87) mais là je n'ai pas eu le temps !!

Halbleiter					
Menge	Typ	Wert	Hersteller	Alternative	Bezeichnung
2	TL084CN		Ti	NS,Mot	I1,I2
1	RC4200ANB		Raytheon		I3
1	LT1044CN8		LT		I4
1	78L05ACP		Mot	Ti,NS	I5
1	79L05ACP		Mot	Ti,NS	
1	BD136		Si,Valvo		T1
8	1N4148,1N914	Ti	alle	D1-D8	
1	B40C800	rund	alle		D9
1	LED gelb	5 mm	alle	alle	D10
1	HLMP4700(LED rot)	5 mm	HP		D11
1	Zener 5% 0.4W	10V	alle		D12

Widerstände					
Menge	Typ	Wert	Hersteller	Alternative	Bezeichnung
2	MBB0207,1%	39	Beyschlag	alle	R17
1	-	100	-	-	R36,39
1	-	330	-	-	R28
2	-	1k	-	-	R30,R37
1	-	2,7k	-	-	R18
1	-	3,9k	-	-	R35
3	-	4,7k	-	-	R20,21,23
2	-	5,6k	-	-	R16,22
1	-	8,2k	-	-	R34
4	-	10k	-	-	R8,19,32,33,34
9	-	22k	-	-	R1,2,6,10,11,12,13,14,15
1	-	33k	-	-	R27
1	-	39k	-	-	R26
1	-	47k	-	-	R7
1	-	51k	-	-	R3
2	-	82k	-	-	R9,R38
1	-	100k	-	-	R25
2	-	220k	-	-	R4,5,29
1	-	300k	-	-	R24
1	-	1M	-	-	R31
3	Cermet 1 G.	10k	DOC	Weston	P1,2,3
5	Cermet 10 G.	5k	-	Bourms	P4,5,6,7,8

Kondensatoren					
Menge	Typ	Wert	Hersteller	Alternative	Bezeichnung
3	EDPU-0,6(2) 100V	100p	Valvo	alle	C15,17,19
14	EDPU-0,6(2) 100V	470p	Valvo	alle	C6,8,10,13,21,27,29,38-42
12	EDPU-0,6(2) 100V	1000p	Valvo	alle	C1-C5,C7,9,11,12,22,28,33
3	EDPU-0,6(2) 63V	0,01u	Valvo	alle	C14,16,18
5	KDPU 50V	0,1u	Valvo	alle	C20,34-37
4	TAG 16V (Tantal)	10u	ITT	alle	C24-26,31
1	TAG 16V (Tantal)	22u	ITT	alle	C23,32
1	EN 12,35 25V(Alu)	100u	ITT	alle	C30

Groß- und Kleinteile					
Menge	Typ	Wert	Hersteller	Alternative	Bezeichnung
1	RuC 100	1 mA	Neuberger	-	H1
1	Rahmen f. RuC100		Neuberger	-	H1 a
1	SBL11 1-3x4		ITT	-	S1
1	SBL11 1-4x3		ITT	-	S4
3	MSTS-101DB	1pol-U	Knitter	-	S3,5,7
1	9080.0101	1pol-U	Marquard	-	S2
1	9080.0201	2pol-U	Marquard	-	S6
2	C93 0802 IC-Sock.	8pol	Ti	alle	So1,2
2	C93 1402 IC-Sock.	14pol	Ti	alle	So3,4
1	C93 1602 IC-Sock.	16pol	Ti	alle	So5
2	71206-050 Buchse	5pol	Hirschm.	-	Bu1,2
1	Stapel 2 Buchse	3pol	Hirschm.	-	Bu3
2	71206-050 Stecker	5pol	Hirschm.	-	Si1,2
1	Stak 2 Stecker	3pol	Hirschm.	-	Si3
3	A16-P Montage-Pl.	16pol	Assmann	alle	MP1,2,3
1	Geh. 2008-1000H		Zeissler	-	
1	Trageb. 2008-3500		Zeissler	-	
1	Al.-Geh. 1061503	1P65	Rose	-	
2	Drehk. 499.40		Mentor	-	
6	NC-Akkus AA	500mAh	Varta	National	
1	Akku-Halter.	6x		alle	
1	Trafo VR1109	9V	Block	alle	
5	Drossel 02036690	1,5Wdg	Valvo	-	
2 m	Kabel LiY(C)Y	5x0,14	Kluxen	alle	
1	Platine doppels.	Europa	DJ9BV	-	DK3LL

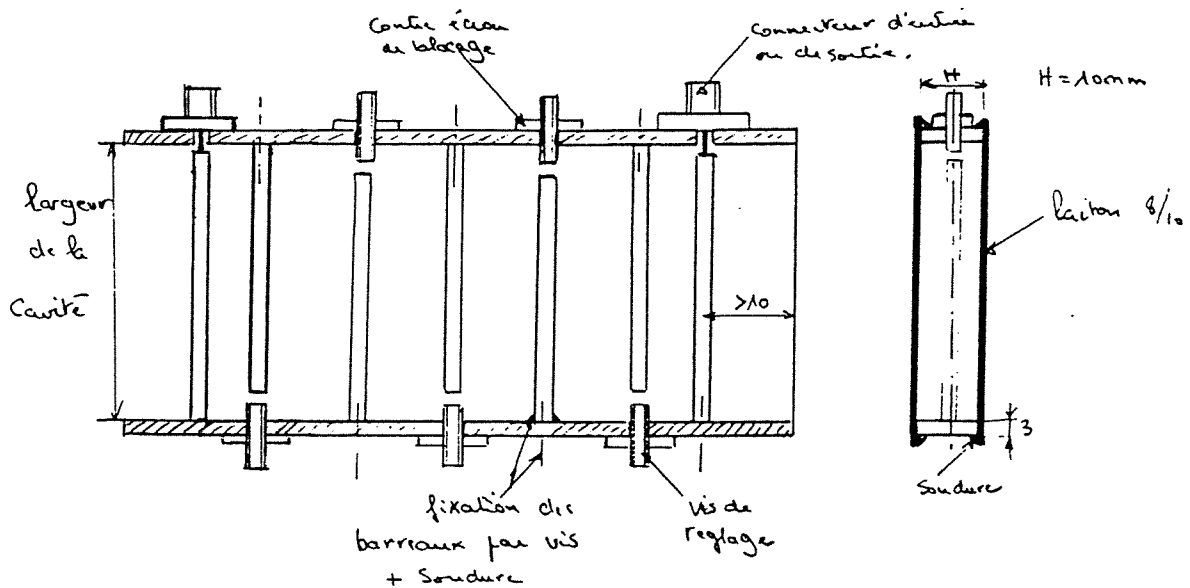

les barreaux sont usés de 1 à 7
Dist CAC est la distance de centre à centre
séparant deux barreaux.

73. FIEHN

Calcul d'un filtre interdigital


F0= 5760.00000 BP= 100.00000 Rip= 0.30000 N= 5

G(1)= 1.481677
G(2)= 1.299208
G(3)= 2.309513
G(4)= 1.299208
G(5)= 1.481677
G(6)= 1.000000

6	0
36.67	0.62
36.67	0.72
36.67	0.58
36.67	0.58

H= 0.009621

ACG(1)= 6.926896	ACM(1)= 0.607102
ACG(2)= 4.705733	ACM(2)= 0.052244
ACG(3)= 5.222403	ACM(3)= 0.041846
ACG(4)= 5.222403	ACM(4)= 0.041846
ACG(5)= 4.705733	ACM(5)= 0.052244
ACG(6)= 6.926896	ACM(6)= 0.607102

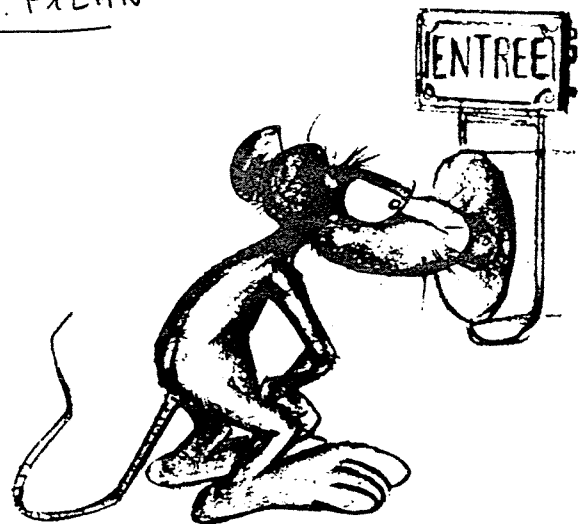

N= 5 H= 10.00000

Número	Diametre/H	Espacement/H	D.C.A.C/H	Diametre	Dist.C.A.C
K	DB0(K)	SBT(K)	C(K)	DBH(K)	CH(K)
1	0.52500	0.49568	0.94818	5.25000	9.48179
2	0.38000	1.24075	1.62575	3.80000	16.25750
3	0.39000	1.31176	1.70176	3.90000	17.01759
4	0.39000	1.31176	1.70176	3.90000	17.01759
5	0.39000	1.24075	1.62575	3.90000	16.25750
6	0.38000	0.49568	0.94818	3.80000	9.48179
7	0.52500			5.25000	

Barreau 2	Longueur=	8.92	Diametre=	3.80mm
Barreau 3	Longueur=	8.82	Diametre=	3.90mm
Barreau 4	Longueur=	8.82	Diametre=	3.90mm
Barreau 5	Longueur=	8.82	Diametre=	3.90mm
Barreau 6	Longueur=	8.92	Diametre=	3.80mm

Largeur de la cavité
(Lambda/4 à F0)

13.02mm

F0=10368.00000


BP= 100.00000

Rip= 0.30000

N= 5

G(1)= 1.481677
 G(2)= 1.299208
 G(3)= 2.309513
 G(4)= 1.299208
 G(5)= 1.481677
 G(6)= 1.000000

3	0
56.01	0.82
56.01	0.72
56.01	0.58
56.01	0.58

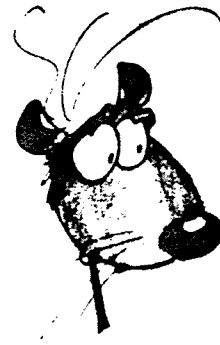

H= 0.005362

Numero Diametre/H

Espace/H

D.C.A.C/H

Diametre

Dist.C.A.C

ACG(1)= 7.079917	ACM(1)= 0.454083	K	DBO(K)	SBT(K)	C(K)	DBH(K)	CH(K)
ACG(2)= 4.897193	ACM(2)= 0.029227						
ACG(3)= 5.300601	ACM(3)= 0.023410	1	0.52500	0.58717	1.04217	5.25000	10.42167
ACG(4)= 5.306361	ACM(4)= 0.023410	2	0.38500	1.42289	1.81039	3.85000	18.10386
ACG(5)= 5.300601	ACM(5)= 0.029227	3	0.39000	1.49301	1.88301	3.90000	18.83009
ACG(6)= 4.897193	ACM(6)= 0.454083	4	0.39000	1.49301	1.88301	3.90000	18.83009
ACG(7)= 7.079917		5	0.39000	1.42289	1.81039	3.90000	18.10386
N= 5	H= 10.00000	6	0.38500	0.58717	1.04217	3.85000	10.42167
		7	0.52500			5.25000	

Barreau 2	Longueur=	3.63	Diametre=	3.85mm
Barreau 3	Longueur=	3.57	Diametre=	3.90mm
Barreau 4	Longueur=	3.57	Diametre=	3.90mm
Barreau 5	Longueur=	3.57	Diametre=	3.90mm
Barreau 6	Longueur=	3.63	Diametre=	3.85mm

Largeur de la cavite
 (Lambda/4 a F0)

7.23mm

FILTRES INTERDIGITES 1296 et 2320 MHz (N°24 Mai 86)

CARACTERISTIQUES TYPIQUES

1296 MHz

Pertes 1,5dB

Rejection OL 1152 75dB

Freq. image > 80dB

→ Dans le cas ou le boitier est
 ferme sur les cotés prévoir
 un espacement plus important sur
 les bords

2320 MHz

Pertes 1,5dB

Rejection OL 60dB

Freq. image 70dB

Quelques exemples de 1296 MHz

F1EHN 1,2dB

F1DED 1,8dB

F1COW 2,8dB

Boitier Fraise trop près
 probleme de parallelisme des
 doigts ???

Pourquoi un transceiver 28 Mhz? :pour une raison bien simple: il sera plus facile de le faire précéder de transverters pour 50,144,432,et même 1296 voire de trafiquer sur 28! tout en réduisant le nombre de modules au strict minimum(un générateur 135-137 très propre n'est pas évident à régler)
Les puristes ne seront peut être pas très satisfaits car un double changement de fréquence nuit toujours à la dynamique, mais de toute façon le résultat est tellement supérieur à n'importe quel appareil Japonnais que l'on peut être rassuré!

Pourquoi ce plan de fréquence? pour une raison pratique, donc, et puis il est toujours possible de réaliser la platine RF pour 144 au lieu de 28, mais on sera désavantagé si l'on veut faire du 432 (un transverter 144-432 est toujours assez vicieux à faire fonctionner)

Bref deux modules principaux: le premier, dans une boîte Schubert 100X160X30 comprend toute la tête HF emission et reception, le mélangeur, le noise-blanker(merci DL7QY) ainsi que la partie F.I. pour la NBFM!!!! désolé les gars, mais BERIC se débrouille pour approvisionner les composants donc il faut un petit argument de vente pour un plus grand nombre de modules! de toute façon, personne ne vous oblige à cabler cette partie.

pour en terminer avec cette partie, sachez que l'on peut compter sur une puissance de sortie d'environ 350 mW et que le récepteur "fait" mieux que 0,4 microvolts, ce qui est de toute façon trop sensible, surtout pour suivre un transverter. Un atténuateur est prévu dans le circuit drain du CF300, les valeurs seront à adapter selon le gout de chacun.


Le second module, de dimension identique, comporte tout le reste: à savoir- l'ampli F.I. SSB/CW


- le détecteur de produit
- le C.A.G.
- l'ampli BF
- le générateur BLU et CW
- le préampli micro
- toute la platine de commande, le relais, le QSK(CW)

Inutile de vous dire que la chose est relativement tassée, bien que tous les composants soient montés à plat.

Il reste donc à l'extérieur:

- le V.F.O. celui ci couvre de 17,3 à 19,3 (la fréquence MF choisie est en effet 10,7 Mhz) le choix de cette fréquence est la conséquence d'essais malheureux avec un VFO 19-21 et une MF 9 Mhz: l'harmonique 2 du VFO (38-42 Mhz moins 9 Mhz redonnait une partie de la bande par battement infradyne, impossible à filtrer de façon satisfaisante)
- éventuellement un compteur, une alimentation secteur, ainsi que différents connecteurs, potentiomètres, commutateurs, etc. mais selon le gout de chacun.

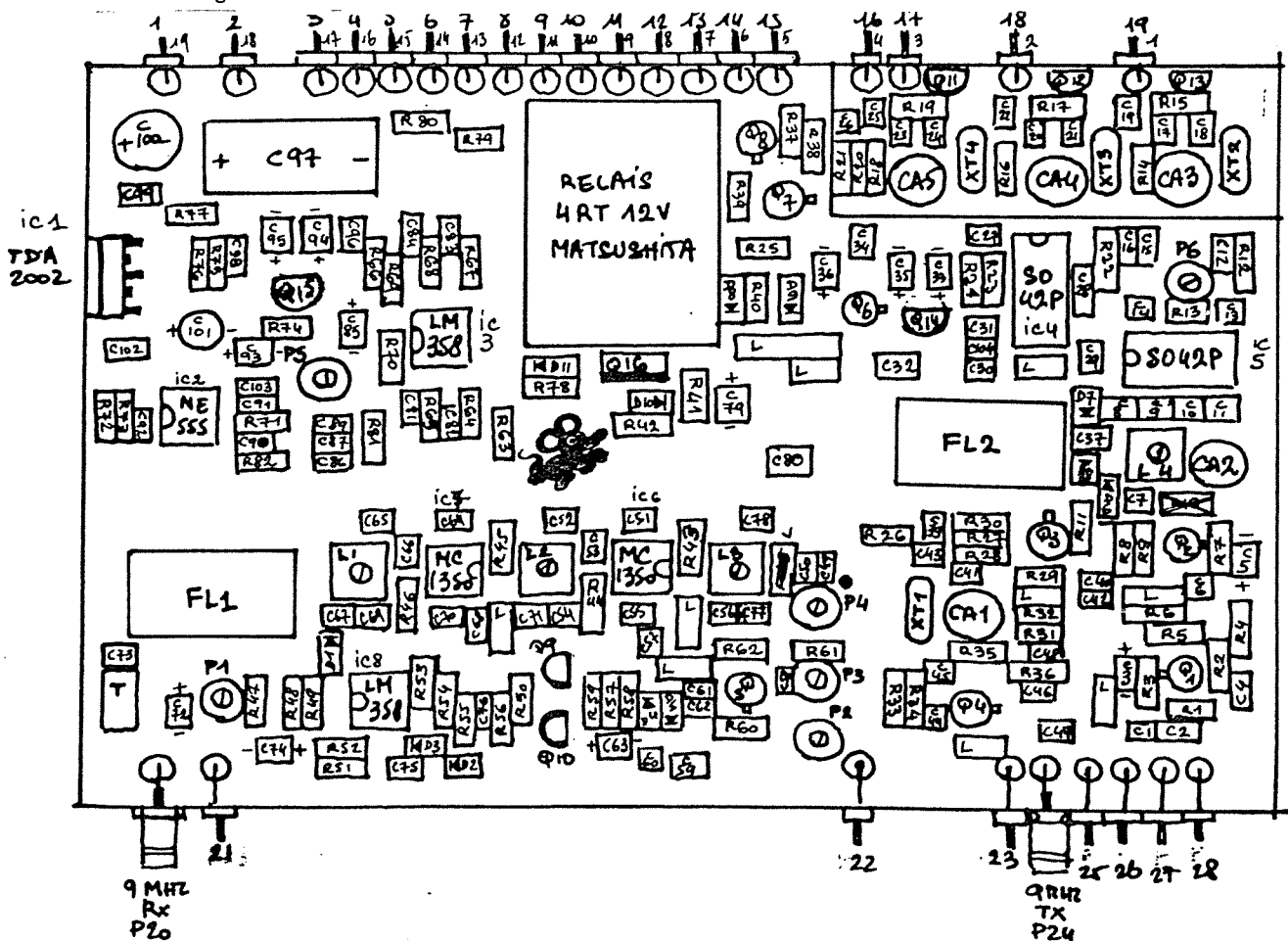


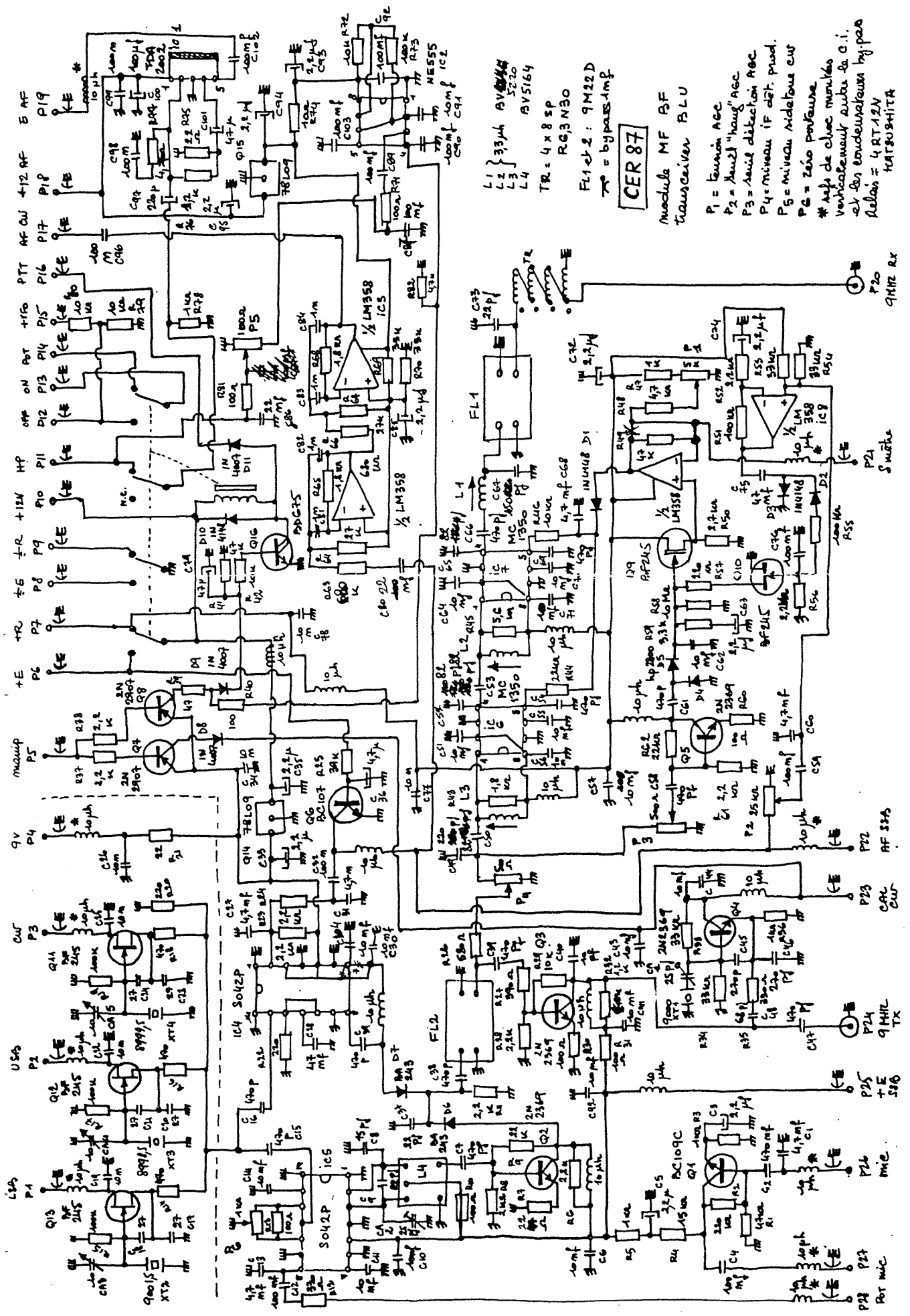


L1 } 33µH AV5164
 L2 } 5220
 L3 }
 L4 } AV5164
 TR = 4 x 8 SP
 RG3 N30
 FL1 et 2 : 9M22D
 = bypass 1mf

CER 87

Module MF BF
Transceiver BLU

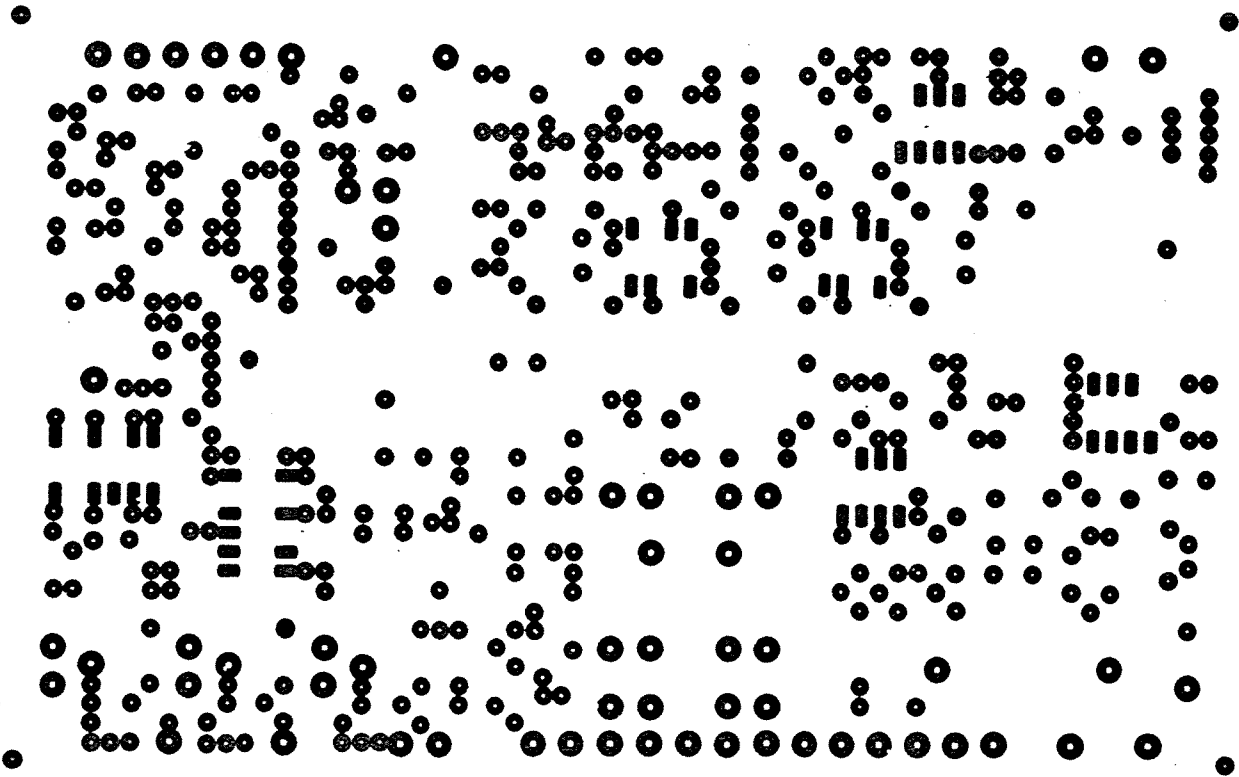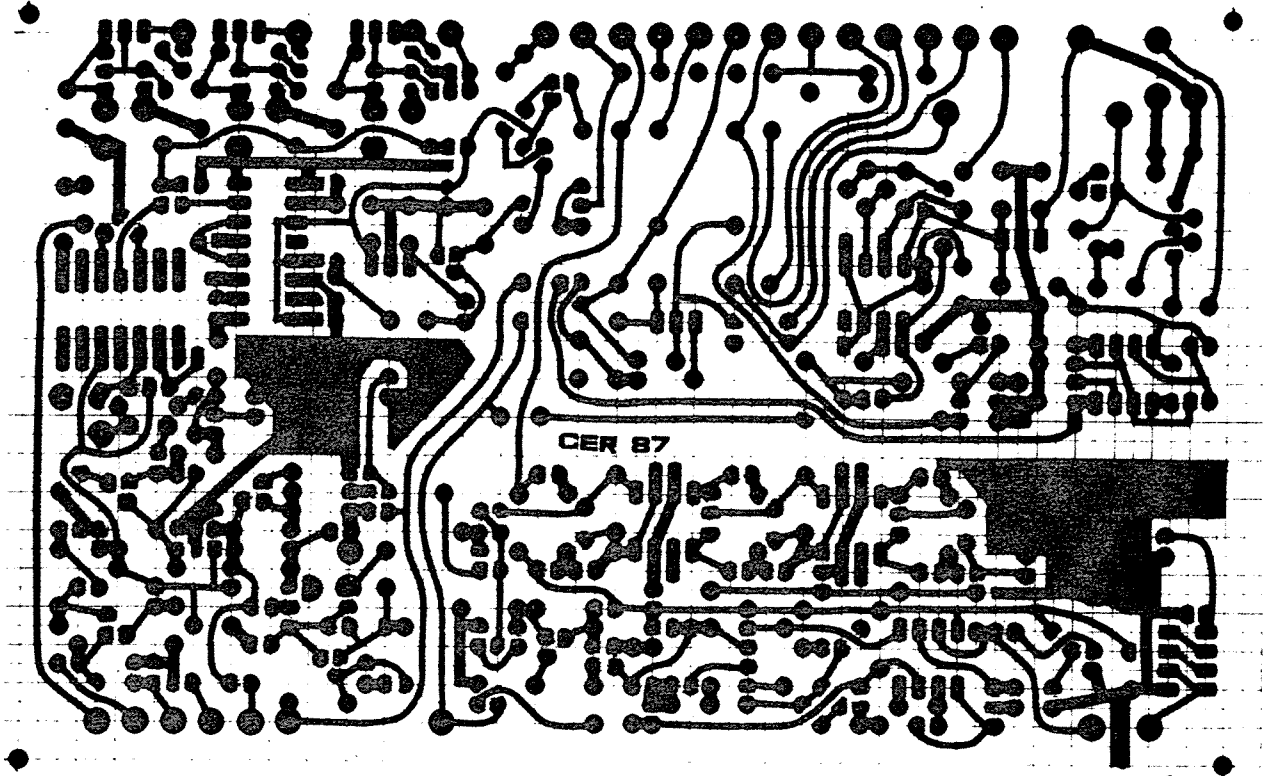- P1 = tension ACC
- P2 = haut "hang" ACC
- P3 = haut détection ACC
- P4 = niveau IF dét. prod.
- P5 = niveau niveau cur
- P6 = zéro porteur
- * Ajust de choc moniteur
- verificateur autre de a.i.
- et les condensateurs by-pass
- Relais = 4 BT-12V
- KATSUBHITA



FILE SUPPLEMENT 05
CER 87
CONTINUED

R1 47k
 R2 220k
 R3 1k
 R4 15k
 R5 1k
 R6 2,2k
 R7 92
 R8 2,2k
 R9 22k
~~R10 100~~
 R11 2,2k
 R12 330
 R13 100 (1/8w *)
 R14 470
 R15 100
 R16 470
 R17 100
 R18 470
 R19 100
 R20 220
 R21 22
 R22 220
 R23 2,2k
 R24 2,2k
 R25 39k
 R26 680
 R27 390
 R28 2,2k
 R29 10k
 R30 100
 R31 100
 R32 2,2k
 R33 33k
 R34 33k
 R35 330
 R36 1k
 R37 2,2k
 R38 2,2k
 R39 47
 R40 100
 R41 47k
 R42 10k
 R43 1,8k
 R44 22k
 R45 5,6k
 R46 10k
 R47 1k
 R48 47k
 R49 47k
 R50 27k

R51 100k
 R52 2,2k
 R53 33k
 R54 33k
 R55 100k
 R56 2,2M
 R57 220k
 R58 10M
 R59 33k
 R60 100
 R61 2,2k
 R62 22k
 R63 680k
 R64 27k
 R65 1,8M
 R66 680k
 R67 27k
 R68 1,8M
 R69 33k
 R70 33k
 R71 100
 R72 10k
 R73 100k
 R74 10
 R75 22
 R76 1200
 R77 47
 R78 1k
 R79 10k
 R80 10k
 R81 100
 R82 47k
 L1 5220
 L2 5055
 L3 5056
 L4 5164
 T R6,3N30
 RLINFL4RT 12V
 FL1 4M22D *
 FL2 9M22D *
 XT1 9001,5 *
 XT2 9001,5 *
 XT3 8998,5 *
 XT4 8998,5 *
 (* on Equivalent
 10,7MHz =
 10M22D;
 10701,5 et
 10698,5

C1 4,7mf
 C2 470mf
 C3 2,2mf
 C4 100mf
 C5 2,2mf
 C6 10mf
 C7 470p
 C8 15p
 C9 282p
 C10 10mf
 C11 10mf
 C12 100mf
 C13 47mf
 C14 10mf
 C15 470p
 C16 470p
 C17 27p
 C18 27p
 C19 10mf
 C20 27p
 C21 27p
 C22 10mf
 C23 27p
 C24 27p
 C25 10mf
 C26 10mf
 C27 47mf
 C28 47mf
 C29 470p
 C30 10mf
 C31 47mf
 C32 100mf
 C33 2,2mf
 C34 10mf
 C35 2,2mf
 C36 47p
 C37 22p
 C38 470p
 C39 470p
 C40 10p
 C41 10mf
 C42 10mf
 C43 10mf
 C44 10mf
 C45 270p
 C46 270p
 C47 470p
 C48 68p
 C49 220p
 C50 22p
 C51 10mf

C52 15p (82p)
 C53 15p (82p)
 C54 470p
 C55 10mf
 C56 10mf
 C57 10mf
 C58 470p
 C59 100mf
 C60 47mf
 C61 470p
 C62 10mf
 C63 2,2mf
 C64 10mf
 C65 15p (82p)
 C66 470p
 C67 150p (150p)
 C68 47mf
 C69 470p
 C70 10mf
 C71 10mf
 C72 2,2mf
 C73 22p
 C74 2,2mf
 C75 47mf
 C76 100mf
 C77 10mf
 C78 10mf
 C79 47mf
 C80 22mf
 C81 1000p
 C82 1000p
 C83 1000p
 C84 1000p
 C85 2,2mf
 C86 22mf
 C87 100mf
 C88 100mf
 C89 100mf
 C90 100mf
 C91 10mf
 C92 100mf
 C93 2,2mf
 C94 2,2mf
 C95 2,2mf
 C96 100mf
 C97 220mf
 C98 100mf
 C99 100mf
 C100 100mf
 C101 47mf
 C102 100mf
 C103 100mf
 C104 10mf

CA1 25p
 CA2 25p
 CA3 10p
 CA4 10p
 CA5 10p
 P1 5k
 P2 25k
 P3 500
 P4 500
 P5 100
 P6 1k
 Q1 AC109C
 Q2 2N2369
 Q3 2N2369
 Q4 2N2369
 Q5 2N2369
 Q6 AC107
 Q7 2N2907
 Q8 2N2907
 Q9 BF245
 Q10 BF245
 Q11 BF245
 Q12 BF245
 Q13 BF245
 Q14 78L09
 Q15 78L09
 Q16 BD675
 IC1 TDA2002
 IC2 NE555
 IC3 LM358
 IC4 8042P
 IC5 8042P
 IC6 MC1350
 IC7 MC1350
 IC8 LM358
 D1 1N4148
 D2 1N4148
 D3 1N4148
 D4 HP2800/FH110
 D5 HP2800/FH110
 D6 BA243
 D7 BA243
 D8 1N4007
 D9 1N4007
 D10 1N4148
 D11 1N4007

- C105, C138: by pass 1mf

DJ9BV 70cm-Yagis

Improved version!

Rainer Bertelsmeier
DJ9BV
Gluecksburger Str. 20
2 Hamburg 50

Revised: 22.12.1987

Copyright © 1987 by R. Bertelsmeier

1. Design Data

Design: DL6WU-Design (Computer simulated and verified)
Design-Frequency: 432.0 MHz (Optimum for SSB-Band 432-434 MHz)
Frequency/Gain characteristic:

Type: DJ9-70-7.7λ


	430	432	434	436	438	440
Gain [dBD]	16.2	16.4	16.5	16.6	16.6	16.5
F/B [dB]	27.5	28.3	28.3	26.6	24.3	22.3

Feed-Point Impedance: 200 Ohm with folded dipole (Typ. VSWR in Figure 1)

2. Mechanical Data

Boom: 20x20x2 mm square aluminium tubing
Elements: 4 mm diameter AlMg3 aluminium rods (i.e. welding rods!)
Driven Element: Folded Dipole 8 mm diameter 8x1 mm Al Tubing (Figure 3)
Balun: 240 mm Teflon cable RG142 B/U (Sleeve length!)
Element-Mount: Nylon rivets 61PR8 from Heyman Manufacturing (Figure 4)


Figure 1 (VSWR curve of DJ9-70-8.5λ):

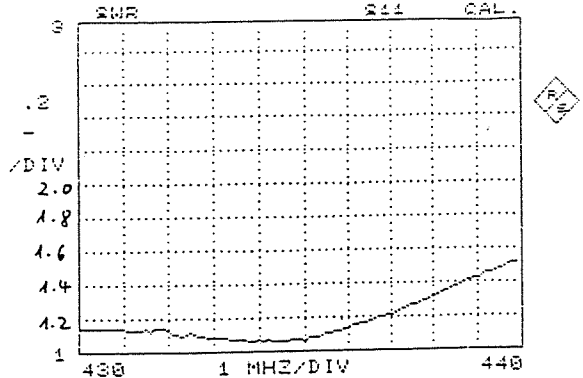

Mechanical Dimensions
(DJ9BV)

Element	Length [mm]	Distance [mm]	Position [mm]	Remarks
R1..R4	400	---	0	4-er Reflector 8 mm Diameter!
DE	325	130	130	
D1	310	55	185	
D2	306	125	310	
D3	302	150	460	
D4	299	175	635	
D5	297	195	830	
D6	294	210	1040	
D7	291	220	1260	
D8	287	230	1490	
D9	287	240	1730	
D10	287	250	1980	
D11	283	260	2240	
D12	283	270	2510	
D13	283	280	2790	
D14	280	280	3070	
D15	280	280	3350	
D16	280	280	3630	
D17	277	280	3910	
D18	277	280	4190	
D19	277	280	4470	
D20	275	280	4750	
D21	275	280	5030	DJ9-70-7.3λ
D22	275	280	5310	DJ9-70-7.7λ
D23	272	280	5590	
D24	272	280	5870	DJ9-70-8.5λ
D25	272	280	6150	
D26	269	280	6430	
D27	269	280	6710	
D28	269	280	6990	DJ9-70-10λ
D29	269	280	7270	
D30	266	280	7550	DJ9-70-11λ

Figure 2 (Reflector arrangement):

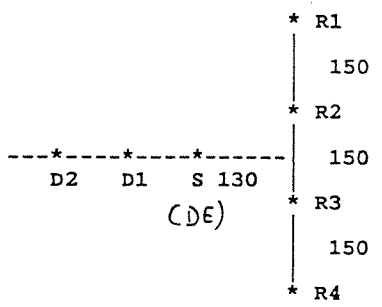

3. Electrical data (@ 432.0 MHz)

Gain figures include 0.1 dB loss for RG142 balun.

Efficiency is typically 98.9 % or 3.2 ° K for antenna without balun.

Electrical data (Simulation by DJ9BV)

Type	Gain [dBD]	F/B [db]	1. Sidelobe [dB]	E-Angle [°]	H-Angle [°]	E-Stack. [m]	H-Stack. [m]
DJ9-70-7.3λ	16.1	24.9	-17.3	23.5	24.5	1.7	1.64
DJ9-70-7.7λ	16.3	28.3	-17.2	23.0	24.0	1.74	1.67
DJ9-70-8.5λ	16.6	23.8	-16.9	22.25	23.0	1.8	1.74
DJ9-70-10λ	17.3	29.5	-16.7	20.9	21.5	1.9	1.86
DJ9-70-11λ	17.5	24.7	-16.6	20.2	20.75	1.98	1.93

Figure 3 (Folded Dipole):



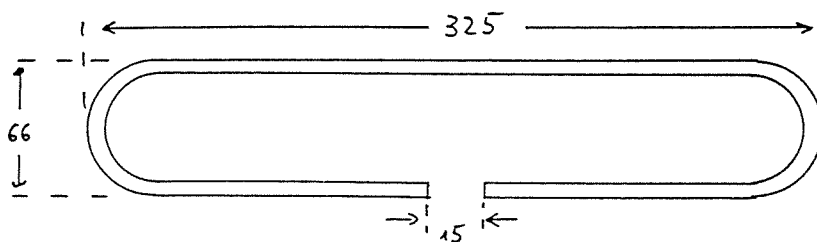


Figure 4 (Element Mounting):

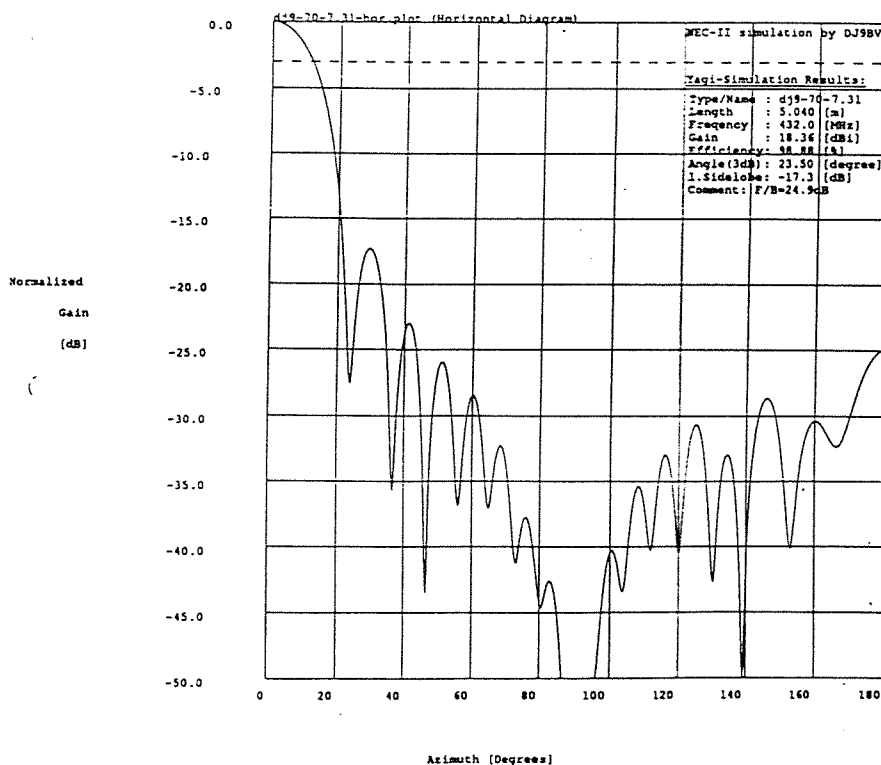

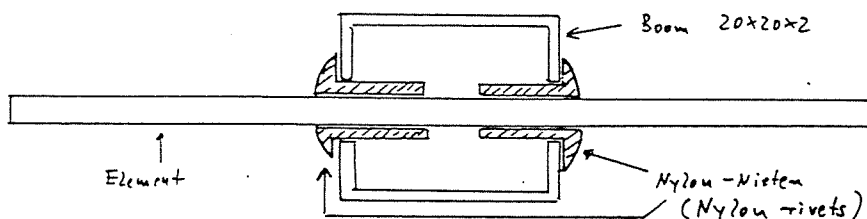

Normalized
Gain
[dB]

