

4) DC Supply for Power Modules

R/C networks are recommended on the bias supply lines, near to the package, to prevent video oscillations which could damage the modules.

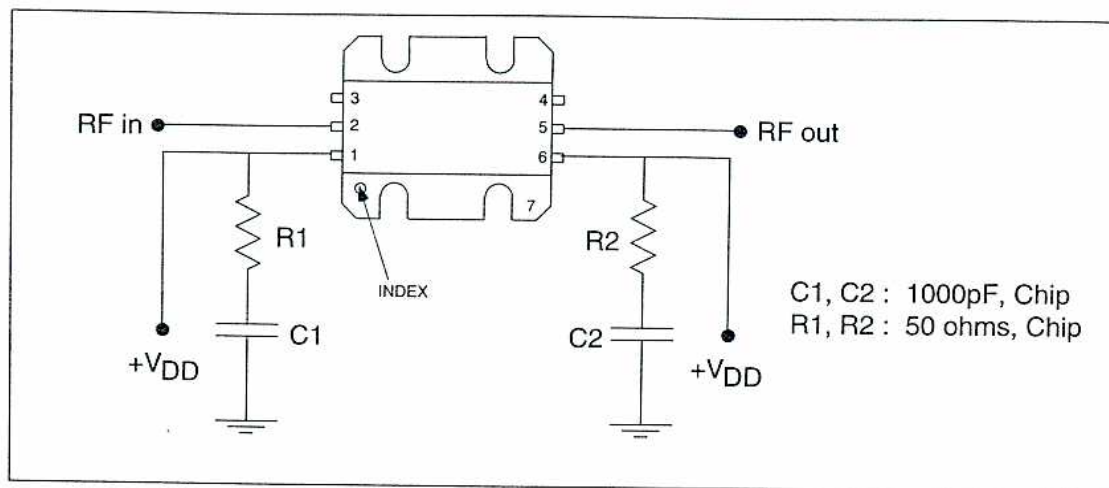


Figure III-4. Single DC Input (e.g. FMC1414P1-02)

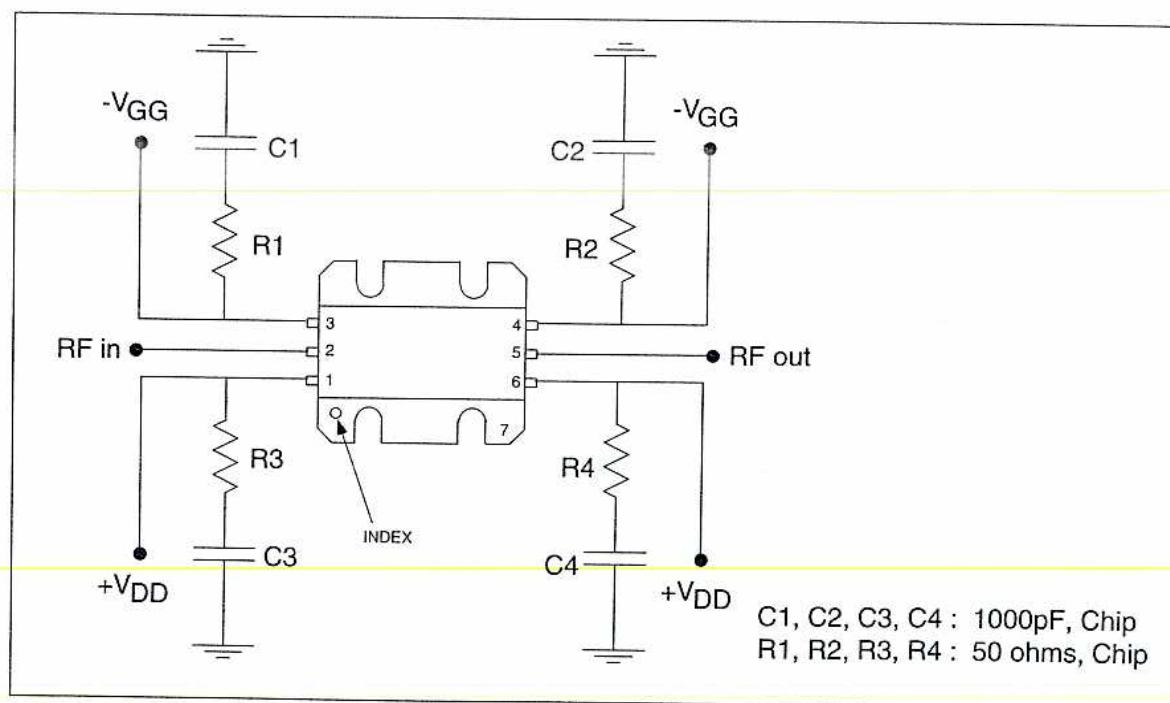


Figure III-5. Dual DC Input (e.g. FMC141401-02)